

DIGITAL SYSTEMS

LAB-6

MUX 4:1 implementation

SHASHI PRABHA

200020043

Aim: Implementation of given SOP using 4:1 MUX

Summary of the experiment:


Implementing 4:1 MUX circuit using **DM74153 Dual 4-Line to 1-Line IC**

Components used:

DM74153 IC, AND gate IC(DM7408) switches, LED, breadboard, power supply, 1k ohm resistor

Design:

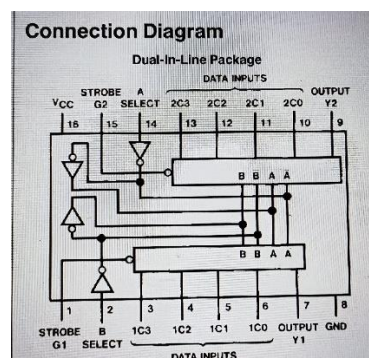Connection diagram of DM74153 IC with it's functional table



Function Table

Select Inputs		Data Inputs				Strobe	Output
B	A	C0	C1	C2	C3	G	Y
X	X	X	X	X	X	H	L
L	L	L	X	X	X	L	L
L	L	H	X	X	X	L	H
L	H	X	L	X	X	L	L
L	H	X	H	X	X	L	H
H	L	X	X	L	X	L	L
H	L	X	X	H	X	L	H
H	H	X	X	X	L	L	L
H	H	X	X	X	H	L	H

Select inputs A and B are common to both sections.
H = High Level, L = Low Level, X = Don't Care


According to this connection diagram we used strobe **G1**

As mentioned to **activate G1** we have to keep it '0' all the time


Now,

we got a question in which we have to implement a 4:1 MUX for the

given SOP

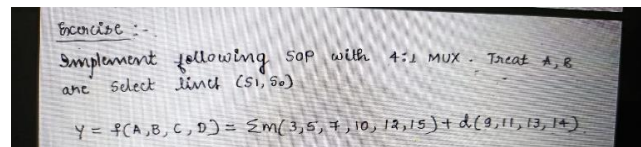


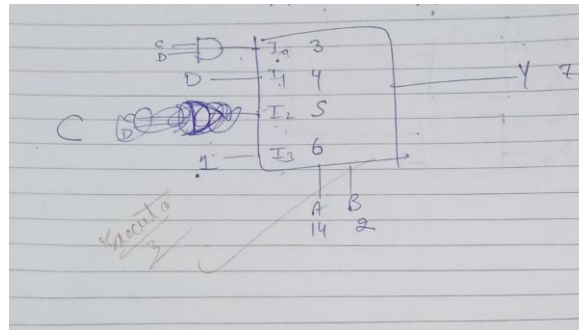Circuit diagram of 4:1 MUX with pin numbers of IC to which it is connected



Here we used one MUX IC and one AND gate.

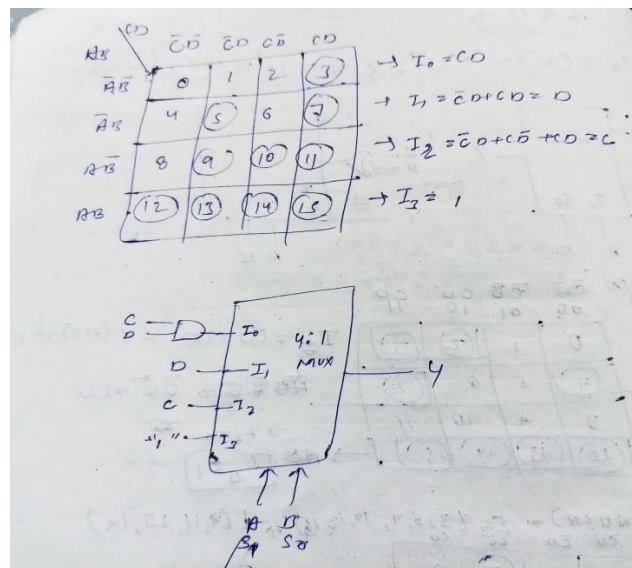Considering A, B as select lines ,
expression for i₀, i₁, i₂, i₃ in terms of C, D are as follows.
Here **we have used don't care** terms to make simplification easier



Here as i₃=1 this implies it will always remain **ON**

I₀=CD , I₁=D , I₂=C , I₃=1

Discussions:

Through out the experiment we discussed many things, like this is the MUX so truth table of 4:1 MUX , circuit diagram of 4:1 MUX ,which strobe should we use, should we use don't care terms, etc and in these discussions we learnt many things.

Conclusion/results:

In this experiment we learnt how to implement 4:1 MUX with given SOP

We learnt how to use 4 inputs to give one output, whom to consider select line whom to inputs. We also learnt how to use strobe in MUX.

And since 3:8 decoder is similar to MUX so with this experiment we also learnt how to implement decoder.

We learnt how to work with a 16 pin IC, as it is quite different with 8/14 pin.