

EE 212 (Electronic Devices Lab)

Experiment-6

Basic Operational Amplifier circuits

Group Info:

1. Manvi Baghel (200020025)
2. Shashi Prabha (200020043)

Objectives: To build inverting amplifier, non-inverting amplifier, differentiator and integrator using Op-Amps

Equipment/Components Required:

1. OP-Amp $\mu A 741$
2. Resistors of suitable values
3. Capacitors of suitable values
4. Regulated power supply
5. Arbitrary Function Generator
6. Digital Storage Oscilloscope

$R_1 = 1k$

$R_2 = 10k$

$R_I = 10k$

$C = 0.01 \times 10^{-6} F$


$R' = 470K$

$R' = 500 k \text{ pot}$

Steps:

Inverting Amplifier

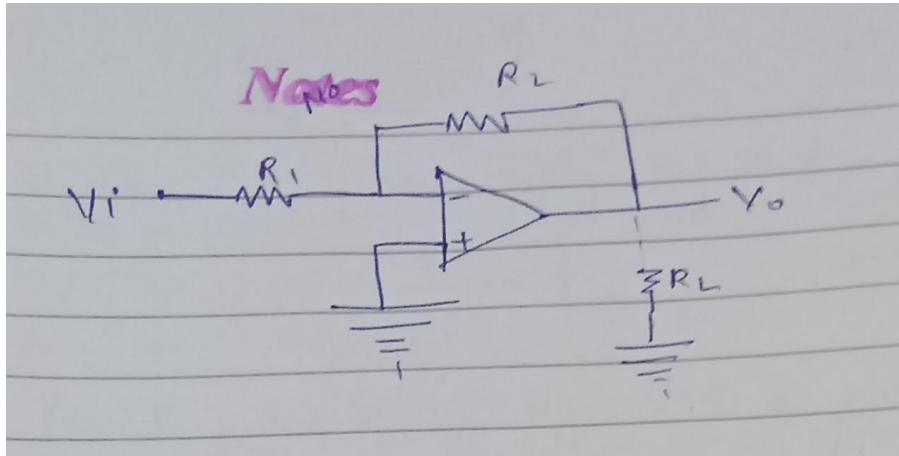
1. First, we wired the amplifier circuit according to the circuit diagram given. We applied a sinusoidal input with a peak of 0.1V and frequency 1 kHz. We observed V_i and V_o on the oscilloscope.



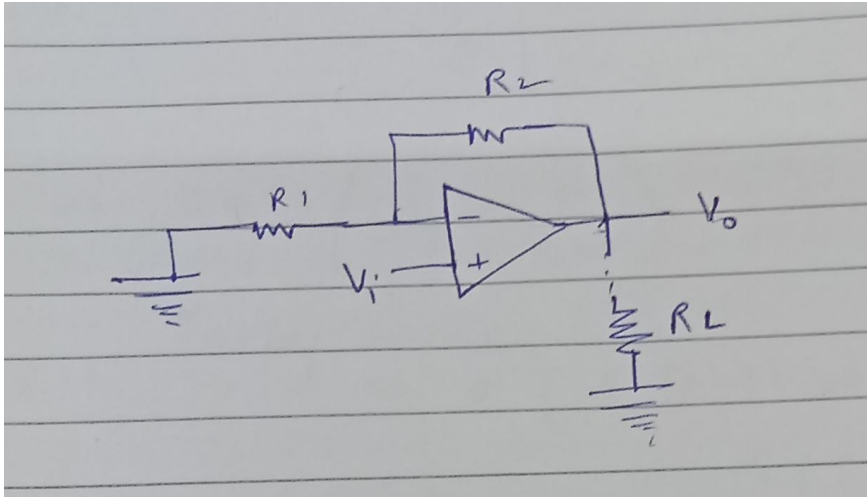2. We increased the input amplitude from 0.1V to 2 V, and observed the output waveform. Explain your observation.
3. We kept the input amplitude at 0.5 V, and increased the frequency until the output waveform became triangular. From the waveform, we calculate the slew rate.
4. We recorded the gain of the amplifier versus frequency for $100 \text{ Hz} < f < 1 \text{ MHz}$.
5. We recorded the frequency response for $R_1 = 1 \text{ k}$, $R_2 = 100 \text{ k}$. We plotted the frequency response for $R_2 = 10 \text{ k}$ and that for $R_2 = 100 \text{ k}$ together.


Non Inverting Amplifier

We repeated all the steps as we did for the inverting amplifier for the new circuit diagram.




Integrator

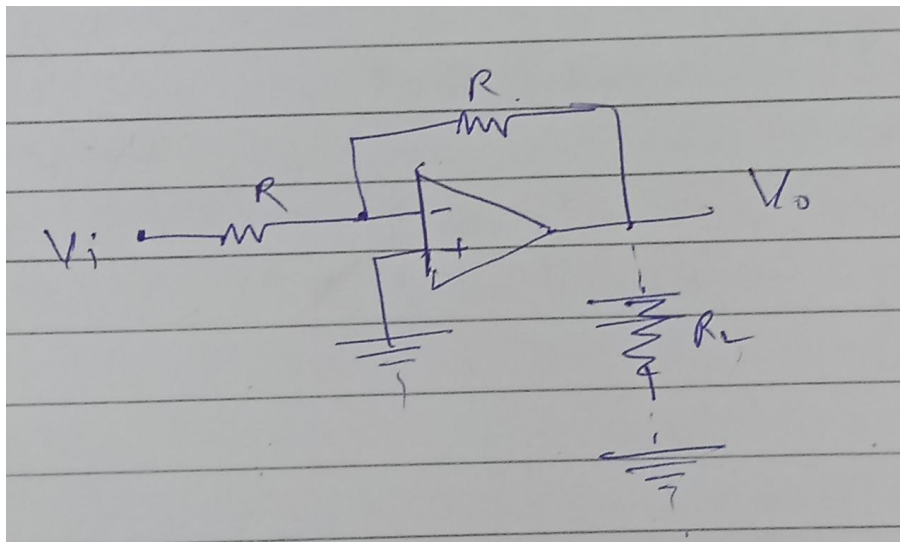1. We wired up the integrator circuit as given in the figure. We gave a square wave input (± 2 V, 1 kHz).
2. We computed the frequency at which an input square wave of ± 2 V produces an output voltage going from -2 V to $+2$ V.
3. We replaced R' with a 500 k pot. Then we changed the pot from minimum to maximum to observe its effect on the output waveform.



Differentiator

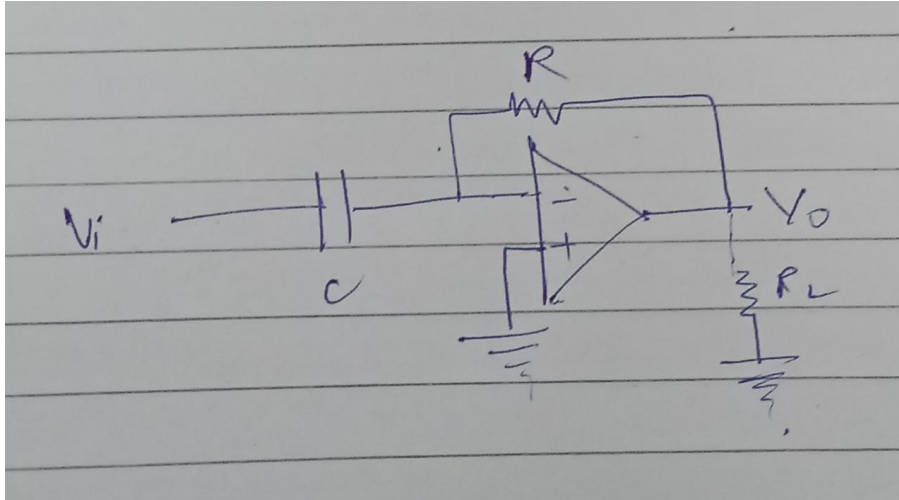
1. We arranged the circuit as shown in the figure with a triangular wave input (± 2 V, 2.5 kHz). We observed $V_o(t)$.
2. We connected a small capacitor $C' = 0.001 \mu\text{F}$ in parallel with R , then observed $V_o(t)$.



Observation

Inverting Amplifier

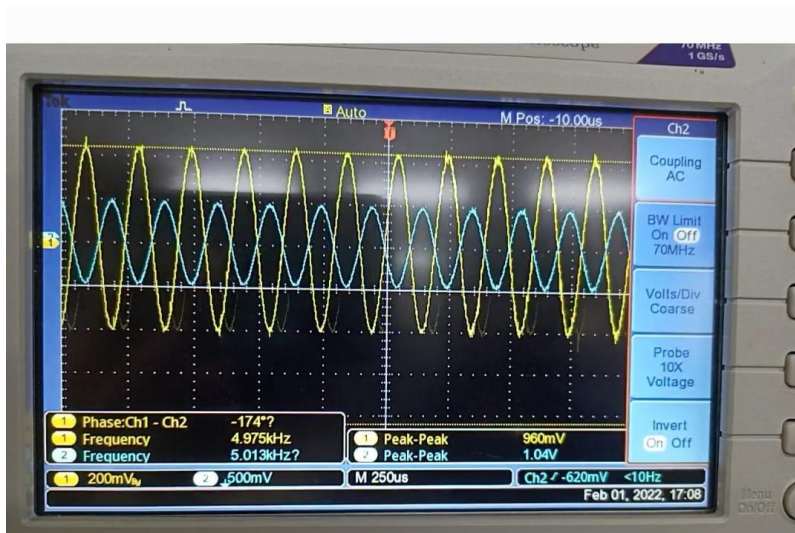1. We observed that the magnitude and phase of V_o was what we theoretically calculated.




Slew rate:

$$\text{Slew Rate} = dV/dt = 2 \cdot \pi \cdot V / (1/f) = 1.7/175k = 0.56V/s$$


Observation Table:

Frequency(in kHz)	Vin	Vout	Gain
0.01	0.5	0.6	1.2
0.02	0.5	1	2
0.05	0.5	2	4
0.1	0.5	3.5	7
0.5	0.5	5.9	11.8
1	0.5	5.95	11.9
2	0.5	5.98	11.96
10	0.5	5.8	11.6
50	0.5	4.3	8.6
100	0.5	2.5	5
250	0.5	1.5	3
500	0.5	0.9	2.5
600	0.5	0.6	2.1
750	0.5	0.5	1.5
900	0.5	0.4	1
1000	0.5	0.35	0.7


Frequency range: 100 Hz to 1 MHz

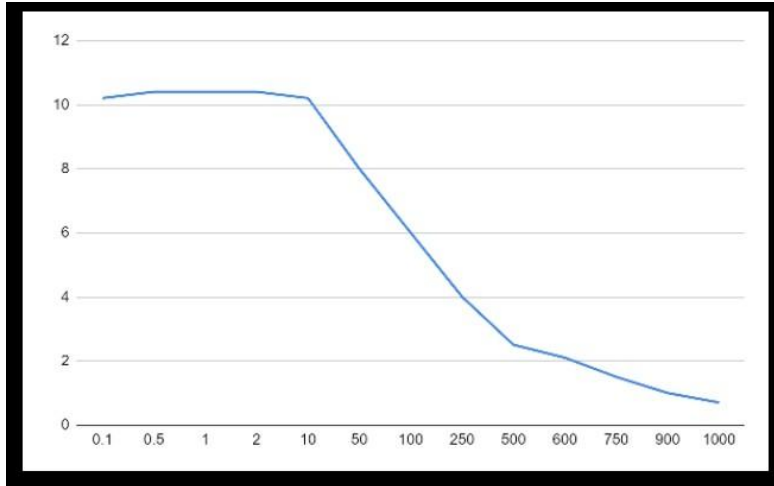


2.

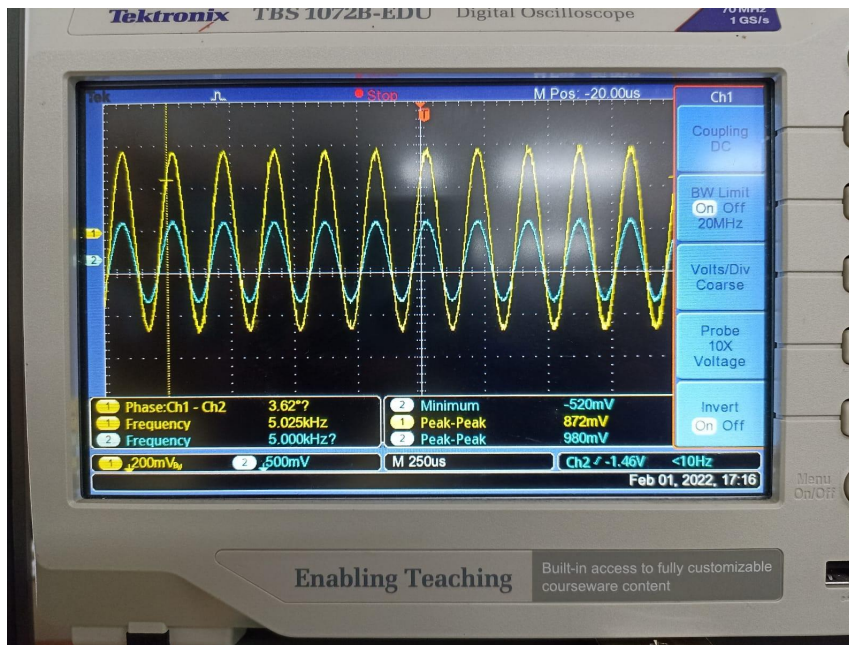

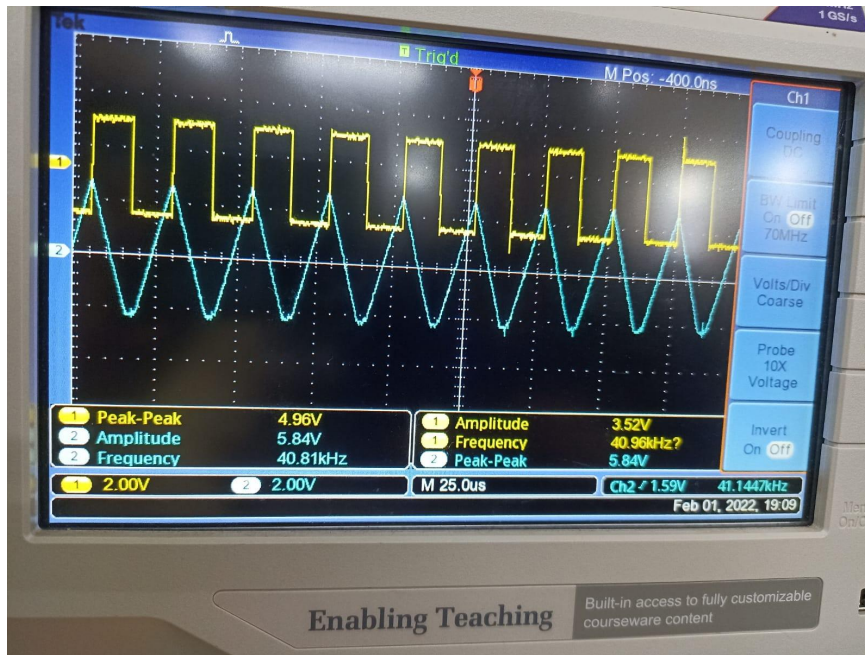3. We got a triangular output for square wave input.
Required frequency:



4.

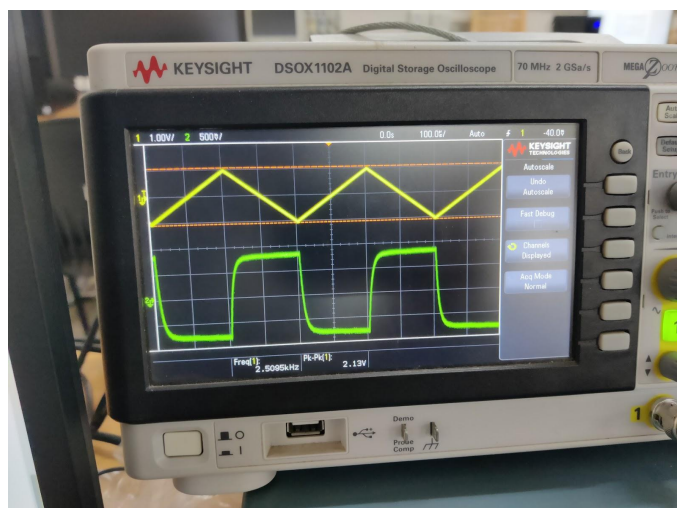

Discussion:

Manvi: We learnt to make circuits of integrator, differentiator, etc for the first time. We even learnt to check a faulty breadboard. We made proper circuits and observed the expected results. It was so informative experience.

Shashi: We learnt how to build inverting amplifier, Non-inverting amplifier, differentiator, integrator using Op-amps practically. And while doing experiment we got the input and output graphs, slew rate, gain of amplifiers as we studied theoretically. With the help of prof. Ruma ma'am we learnt how to check shorted breadboard and grounding wire. Overall it was a nice experiment and we learned a lot through the experiment.