

## **EXP 03- DESIGNING OF INDUCTOR AND MEASURING INDUCTANCE**

Report by:

*Shivam Kumar(200020044)*

*Shashi Prabha(200020043)*

### **AIM:**

DESIGNING OF INDUCTOR AND MEASURING INDUCTANCE


### **COMPONENT USED:**

- TL494 PWM Controller with IC Base
- Resistors - a)  $47\text{k}\Omega$ ,  $4.7\text{k}\Omega$ ,  $10\Omega$ ,  $1\text{k}\Omega$  ;  $0.25\text{W}$  b)  $150\Omega$ ;  $2\text{W}$
- Rheostat ( $50\text{k}\Omega$ ;  $10\text{k}\Omega$ )
- Circuit of Uncontrolled Rectifier (using LM317 or IC7815)
- Shorting pins
- Capacitor( $100\text{nF}$ ,  $10\text{nF}$ ,  $100\text{nF}$ )
- Inductor  $1.2\text{mH}$
- Diode FR107
- MOSFET IRF540
- PCB Board
- Wires(M & F), Wire stripper
- Regulator IC 7815 & LM317
- Soldering Equipment
- Oscilloscope
- Regulated Power Supply


### **SUMMARY:**

In this experiment we are using designing inductor and then measuring its inductance.

## CIRCUIT DIAGRAM:

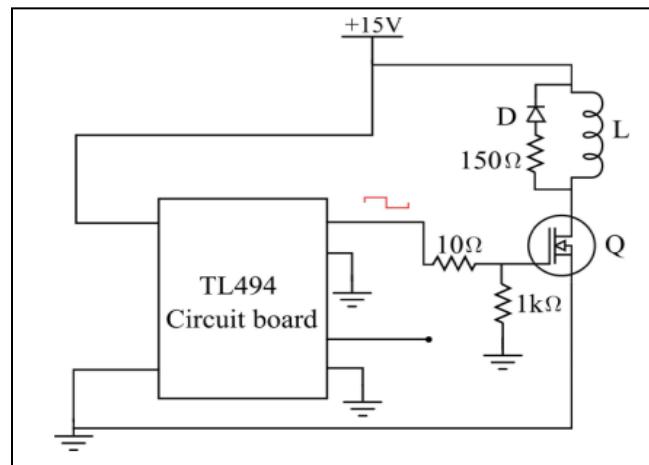

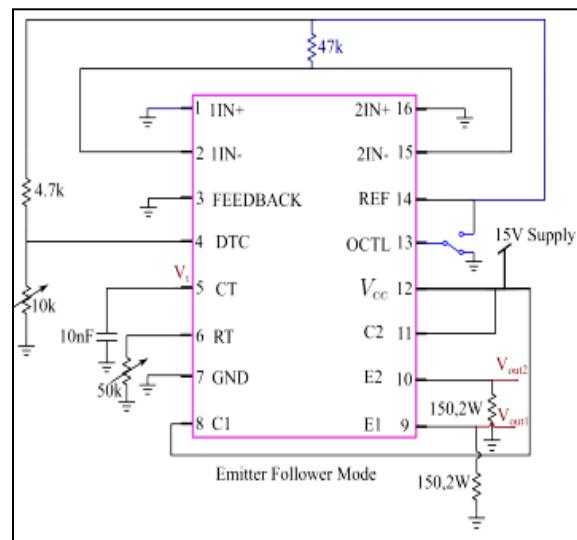**Fig(a):** Circuit diagram for connecting TL494 with the inductor in single-ended supply.




**Fig(b):** Connection diagram of TL494 to work as in emitter follower mode with single-ended supply
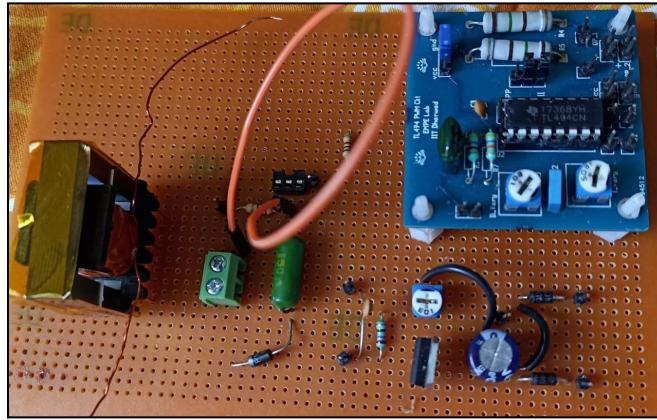
## PROCEDURES:

- Focusing on the necessary calculations, we designed the inductor specifications, then we did confirmation for the inductance value.
- Tested the inductance value by winding the inductor using the "Linear Coil And Toroidal Winding Machine."

- We built the circuit in PCB as shown in the above diagram of fig.(a) to calculate the inductance of the inductor.
- The whole circuit of PCB looked like this after connecting the inductor of unknown inductance(L) and TL494 PCB:



- Have used the TL494 PWM generator that was previously designed for applying the gate pulses:
  - With 50% of the duty cycle at a frequency of 10 kHz.
  - Isolated the mosfet gate while adjusting the TL494 PWM pulses.

Snapshot of TL494 used while this exp. in the single-ended mode for emitter-follower connection of mosfet:




- Measured the drain-source voltage and drain current once the TL494's pulses have been set by connecting the gate pulses to the measuring circuit.
- At the beginning and end, we measured the rise time of the drain current.
- Obtained the gate pulse and inductor current as shown in fig.(d)
- After getting the output waveform of the inductor current shown in fig.(d), we calculated the value of the inductor using the equation:

$$L = \frac{V\Delta T}{\Delta I}$$

- Note: Only once the driver is attached to the MOSFET's gate terminal then we should turn ON the power supply.

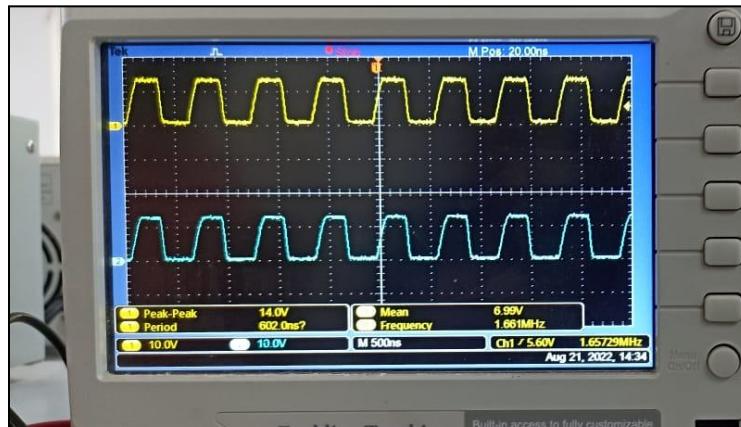
## RESULTS AND OUTPUTS:

- The output PWM produced by the TL494's emitter follower circuit in single-ended power supply mode.




**RESULT:** Fig.(c) We obtained an emitter follower waveform in single-ended mode with a duty cycle in the range of 50% and frequency around 50kHz.

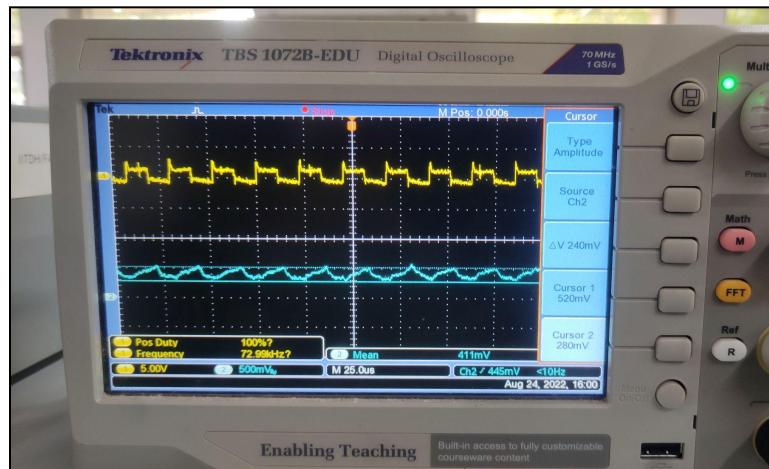- After utilizing these pulses to the circuit as shown in fig.(a), we observed the pulse of MOSFET'S gate terminal and also the current output across the inductor as a triangular waveform:



**RESULT:** Fig.(d) We obtained the gate pulses with a mean voltage of 5V in the form of square signals and triangular waveform of the inductor current. Then, we calculated the peak-to-peak current of the inductor waveform and calculated ( $L \approx 1.38\text{mH}$ ) using the equation:

$$L = \frac{V\Delta T}{\Delta I}$$

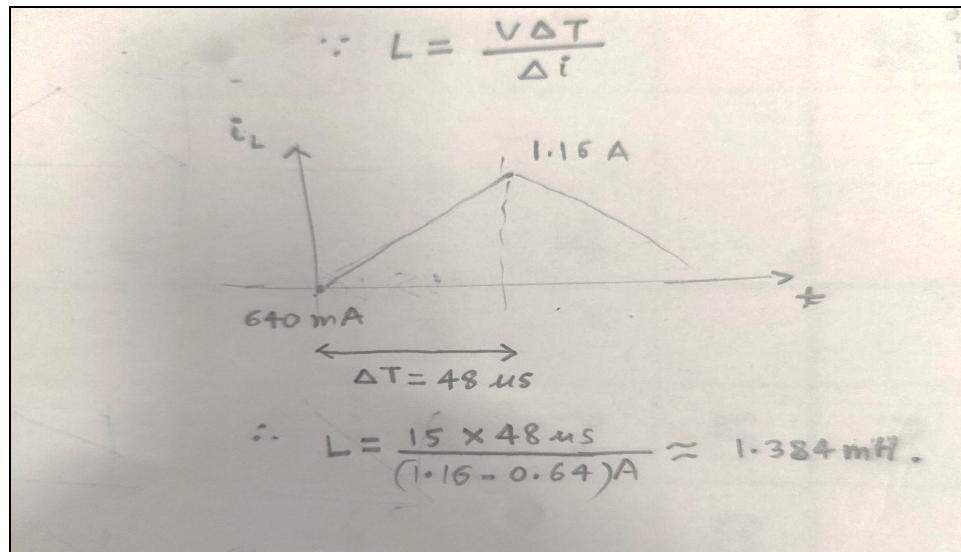


- After theoretically calculating the inductance value ( $L \approx 1.384\text{mH}$ ), we again checked the inductance (L) using an LCR meter with shown value:



**RESULT:** LCR meter clearly shows that the wound inductor which we implemented in the circuit has an inductance value of **1.44880mH** close to the theoretical value of **1.384mH**.


## ANALYSIS:

- The characteristics of voltage and current across the inductor branch of the circuit (fig.a) can be explained as shown:

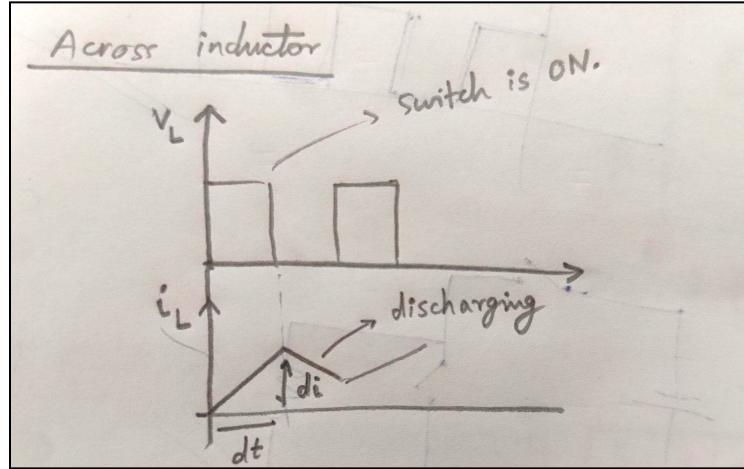


**Fig.(e)** We can clearly see the discharging of the inductor through the free wing path when the pulse is going OFF.

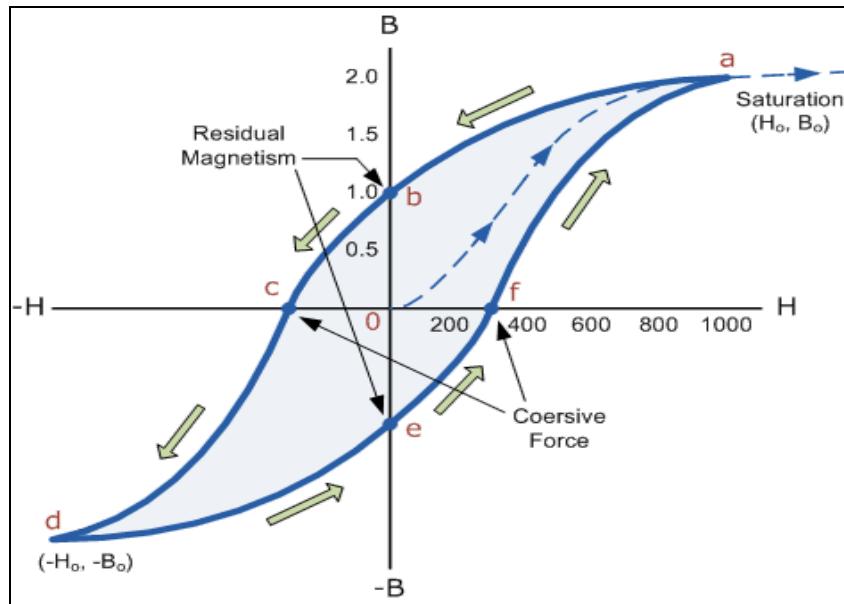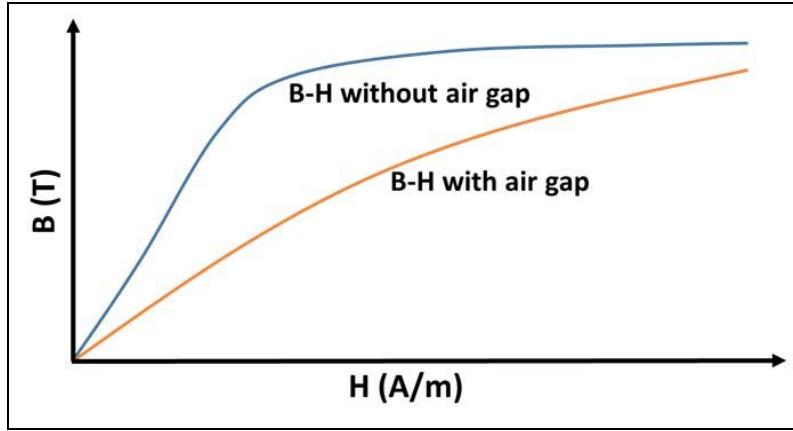- B-H curve for the inducting element can be shown in the below figure:




**Fig(f):** Hysteresis loop shows the dependency of applied current ( $H=\mu I$ ) with the magnetic field ( $B$ ).



**Fig(g):** The B-H curve with a specific air gap can reduce the energy loss as we can see the area of the curve is lesser in an air-gapped inductor. In our experiment, we took the air gap of  $2mm^2$  in each connecting section of the inductor loop.

"Area of the hysteresis loop of any substance represents energy loss in magnetizing a substance."

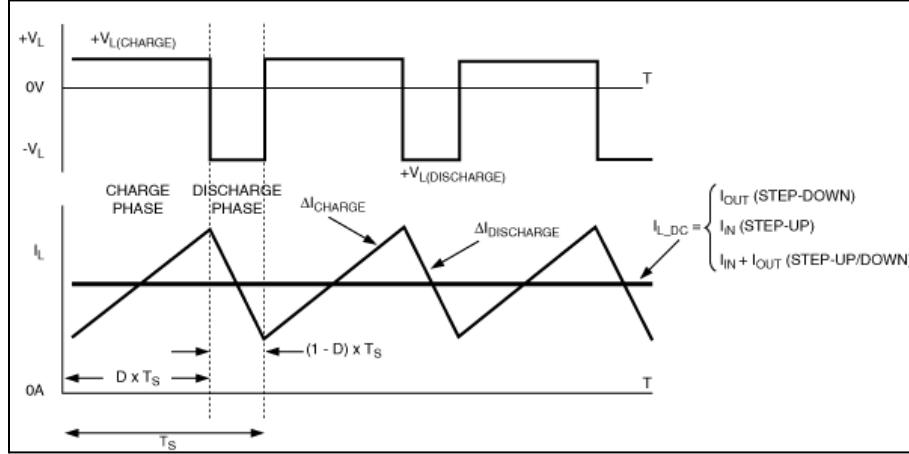- ❖ In this exp. we are using the inductor, which stores energy and supplies energy to the circuit to maintain current flow during “off” switching periods of TL494 SMPS supply.



- ❖ Magnetic field is caused by the current as [  $B = \frac{\mu_o NI}{l}$  ], “inductor” resists the change in the current wrt. Faraday’s law:

$$[ E_L = -d\phi/dt ] = -d\left(\frac{\mu_o N^2 IA}{l}\right)/dt = -\left(\frac{\mu_o N^2 IA}{l}\right) = -L\left(\frac{di}{dt}\right); \text{ where } L = \frac{\mu_o N^2 A}{l}$$